



Done By:

Marwan Bitar 4110259 Abdulsalam Kanjou 4110002

Instructor:

Dr. Ahmed Mechraoui

December – 2021




















Multisim Simulation Development Suggestions
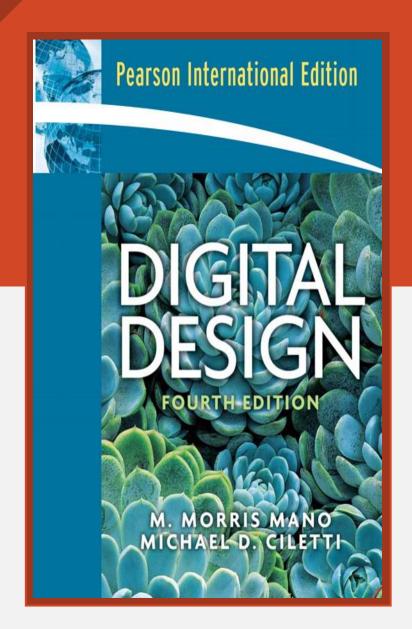
# Introduction

- In this project we wanted to create a smart home control system that is easy to use and set-up.
- > Using the knowledge we gained throughout this course, we were able to make this simple system with logic gates.





**Theory** 

#### We have three inputs:

- 1- Door button (Lock).
- 2- Time.
- 3- Temperature.





- 1- Lights.
- 2- AC.
- 3- Curtains.
- 4- Coffee maker.







#### Truth Tables & K-maps

Inputs			Outputs			
Door Button	Time	Temp	Lights	AC	Curtains	Coffee Maker
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	0	1	1	1	0	0
1	1	0	0	0	1	1
1	1	1	0	1	1	1

Door Button = X, Time = Y				
Lights (K-map)				
X\Y	0	1		
0	0	0		
1	1	0		
Lights = XY'				

Door Button = X, Time = Y			
Curtains (K-map)			
X\Y	0	1	
0	0	0	
1	0	1	
Curtains = XY			


Door Button = X, Time = Y, Temperature = Z				
AC (K-map)				
X\YZ	00	01	11	10
0	0	0	0	0
1	0	1	1	0
AC = XZ				


Door Button = X, Time = Y			
Coffee Maker (K-map)			
X\Y	0	1	
0	0	0	
1	0	1	
Coffee Maker = XY			

#### The Function Table of the Door Lock

Save	Code0 to Code4 (any combination)	<b>Door Button</b>
0	X	0
1	A specific combination	1
0 or 1	The same combination	1
0 or 1	A different combination	0


#### Multisim Simulation

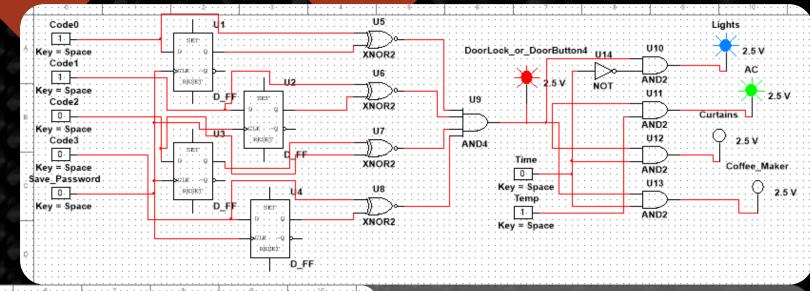


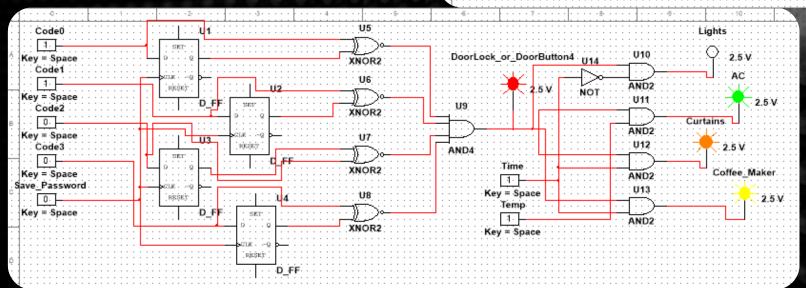


DEL


# Hardwired Components

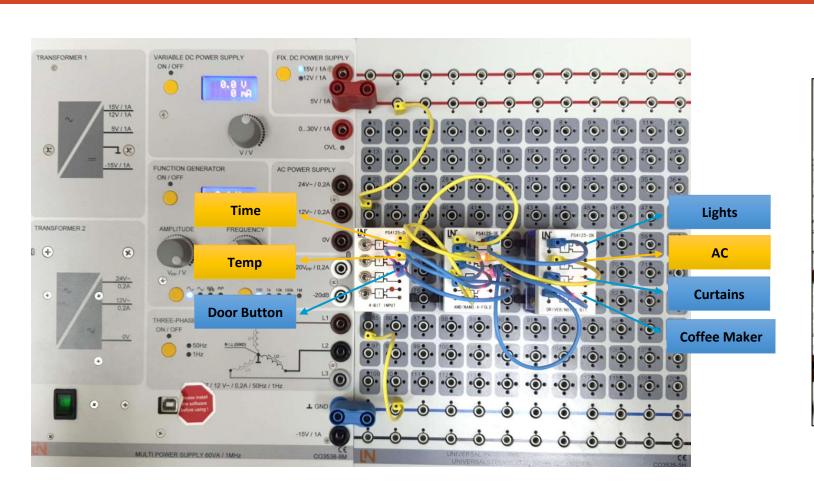

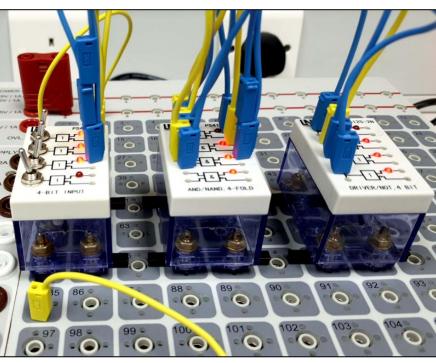

## Tinkercad Simulation

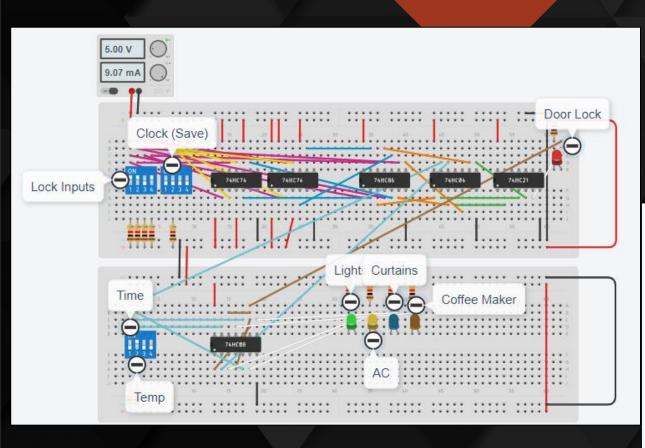

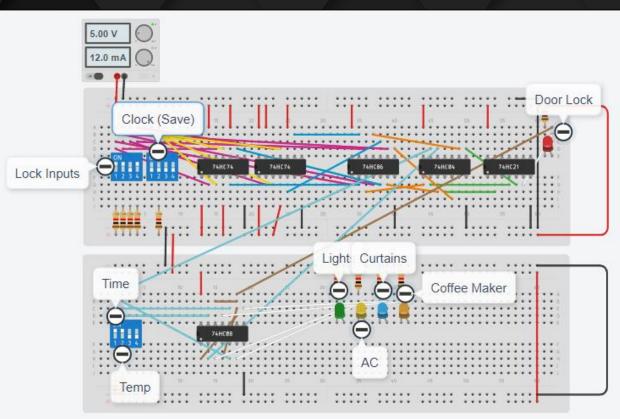

# Development Suggestions

1- Replace the Time input with a timer.



2- Add extra outputs.



3- Include more inputs.



### Conclusion

• The implementation of our EE231 course.



The future improvement.



## THE END



# Any Questions?

